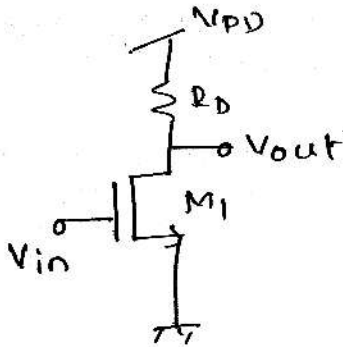


PESIT-BSC

Dept. of ECE

1st - Test (scheme and solution)
 (M.Tech. 2nd SEMI). SUB: AMVD.
 Faculty: Kunalichav. S

D.a.



$$V_{out} = -g_m \cdot R_D \cdot V_{in}$$

OR

$$V_{out} = V_{DD} - I_{Dsat} \cdot R_D$$

$$\therefore V_{in} - V_{TH} = V_{DD} - I_{Dsat} \cdot R_D$$

$$= 10 - \frac{1}{2} (10^{-4}) \cdot (V_{ov})^2 \cdot 10^5$$

$$\therefore V_{ov} = 1.3177V = V_{in} - V_{TH}$$


$$\therefore V_{in} = \underline{\underline{2.734}}$$

\therefore Range is $\boxed{1.42V \leq V_{in} \leq 2.734}$

- (8M)

(2) second order effects of in MOS device
 (Refer class-notes) $\rightarrow 04 \times 02M \rightarrow$ (8M)

(2) $A_v = \frac{-g_{m1}}{g_{m2}}$

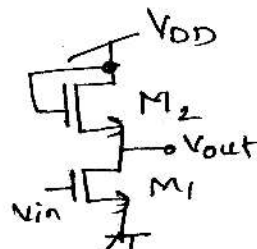

$\therefore I_{D1} = I_{D2} \Rightarrow A_v = \left(\frac{V_{GS2} - V_{TH2}}{V_{GS1} - V_{TH1}} \right)$

(P. 50)


$$\frac{V_{GS2} - V_{TH2}}{V_{GS1} - V_{TH1}} = \sqrt{5}$$

8M

$$V_{in} = 1.41V$$


→ To keep the device sat the edge of the triode region.

4

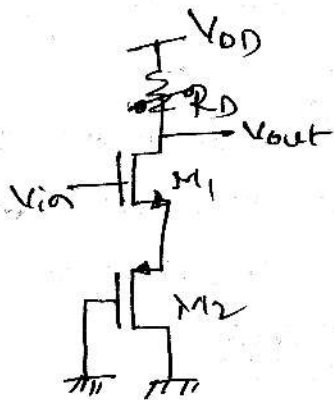

M₂ is diode connected hence the impedance is $\frac{1}{g_{m2}}$

The small signal model is

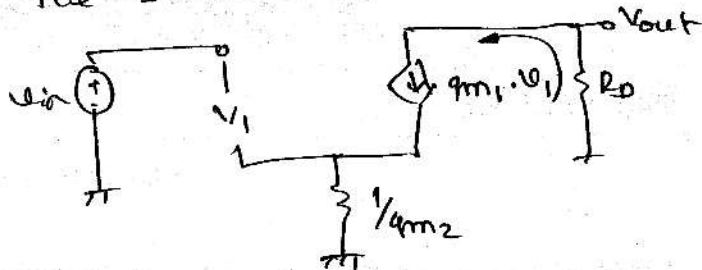

$$A_v = \frac{-g_{m1} R_D}{1 + \frac{g_{m1}}{g_{m2}}}$$

8M

5 ID expression of MOS device, (refer class notes)

$$I_D = \mu_n \cdot C_{ox} \cdot \frac{W}{L} \left\{ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right\} \rightarrow \text{L.R.} \quad (3M)$$

$$I_D = \frac{1}{2} \mu_n \cdot C_{ox} \cdot \frac{W}{L} (V_{GS} - V_{TH})^2 \rightarrow \text{S.P.} \quad (3M)$$

$$g_{m1} = \mu_n \cdot C_{ox} \cdot \frac{W}{L} (V_{GS} - V_{TH}) \rightarrow \text{S.P.} \quad (1M)$$

$$g_m = \mu_n \cdot C_{ox} \cdot \frac{W}{L} \cdot V_{DS} \rightarrow \text{L.R.} \quad (1M)$$

page-02