


USN	1	P	E							
	PESIT Bangalore South Campus Hosur road, 1km before Electronic City, Bengaluru -100 Department of Electronics and Communication VLSI Design and Embedded Systems									

INTERNAL ASSESSMENT TEST 2		
Date	: 03/04/2017	Marks: 40
Subject & Code	: VLSI Testing – 16EVE22	Specialization : VLSI & EMB
Name of faculty	: Prof. Ananda M	Time : 8:30am -10:00am
Note: Answer FIVE full questions, selecting any ONE full question from each part.		Marks
PART 1		
1	List test Generation Techniques for Combinational circuit and explain Fault Matrix method?	8
2	What is D-Algorithm? List the types of Cubes? Write the Singular Cubes and Propagation D-cube for two input Nor Gate?	8
PART 2		
3	Explain the basic principle of Path Sensitization method to detect the fault in the circuit?	8
4	What is Primitive D-cube of a fault? Write Pdcf for all single stuck-at faults for the three-input NAND gate?	8
PART 3		
5	What is BIST? Explain the Partitioning of a circuit for autonomous testing with an Example ?	8
6	What is BILBO? with Logic diagram of a BILBO explain BILBO-based BIST Architecture ?	8
PART 4		
7	Explain D-algorithm method to generate a test for a given fault with the test generation process steps for detecting $\alpha(s-a-1)$ fault in Figure 7 below.	8
8	What is PODEM? With steps Illustrate the application of PODEM by deriving a test for fault $l\ s-a-1$ in the circuit shown in Figure 8 below	8
PART 5		
9	Explain the basic principal of Boolean Difference with examples.	8
10	Explain the compression techniques for Output Response Analysis.	8

 


Figure 7 for Question 7

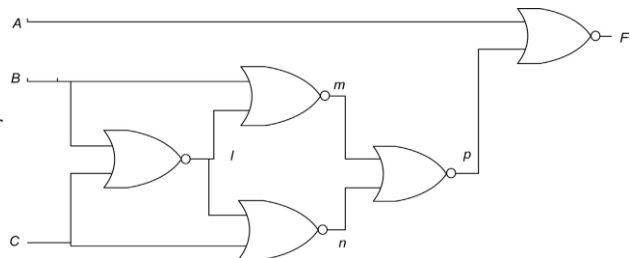



Figure 8 for Question 8

USN	1	P	E							
	PESIT Bangalore South Campus Hosur road, 1km before Electronic City, Bengaluru -100 Department of Electronics and Communication VLSI Design and Embedded Systems									

SCHEME AND SOLUTION
SECOND INTERNAL TEST

Q.N 0	Note: Answer FIVE full questions, selecting any ONE full question from each part.	Marks
PART 1		
(1)	Test Generation Techniques for Combinational circuit- 4 types-2 marks → refer Text 1 Explaining the Fault Matrix method with circuit and truth table- 6marks → refer Text 1 Total= 2+6=8	8 marks
(2)	D-Algorithm – definition → 2 marks → refer Text 1 List the types of Cubes → 1 marks → refer Text 1 Writing the Singular Cubes and Propagation D-cube for two input Nor Gate: 5 marks → refer slides. Total= 2+1+5=8	8 marks
PART-2		
(3)	The basic principle of Path Sensitization method to detect the fault in the circuit : Text 1 → Explanation 2 marks Circuit diagram : 2marks and 6 steps → 4 marks Text 1 Total= 2+2+4 =8	8 marks
(4)	Primitive D-cube of a fault definition → 2 marks → Text 1 Writing Pdcf for all single stuck-at faults for the three-input NAND gate Circuit diagram → 2 marks, explanation → 4 marks Total= 2+2+4 =8	8 marks
PART 3		
(5)	BIST definition- 2 marks → Text1 The Partitioning of a circuit for autonomous testing with an Example Circuit diagram → 3 marks and explanation → 3 marks Total= 2+3+3=8	8 marks
(6)	BILBO definition → 2 marks → Text1 Logic diagram of a BILBO → 3 marks Explaining BILBO-based BIST → 3 marks Total= 2+3+3=8 marks	8 marks
PART 4		



PESIT Bangalore South Campus

Hosur road, 1km before Electronic City, Bengaluru -100

Department of Electronics and Communication
VLSI Design and Embedded Systems

(7)

D-algorithm method to generate a test for a given fault with the test generation process steps for detecting α (s-a-1) fault in Figure 7 below.

 


Figure 7 for Question 7

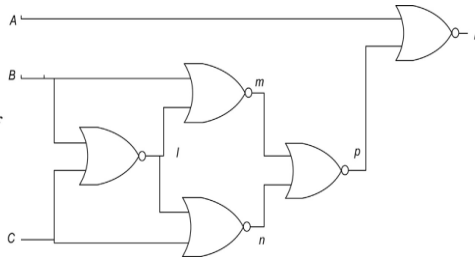


Figure 8 for Question 8

8 marks

Rewriting the circuit diagram Figure: \rightarrow 2 marks
six steps for solving the circuit \rightarrow 6 marks

Total= 2+4=8

(8)

PODEM definition \rightarrow 2 marks \rightarrow Text1
Rewriting the circuit diagram Figure: \rightarrow 2 marks
With steps Illustrate the application of PODEM by deriving a test for fault 1 s-a-1 in the circuit shown in Figure 8 \rightarrow 4 marks

Total= 2+2+4=8

8marks

PART 5

(9)

The basic principal of Boolean Difference with examples \rightarrow Explanation with equations
 \rightarrow 4+4 marks

Total= 4+4=8


8 marks

(10)

The compression techniques for Output Response Analysis
3 techniques \rightarrow 1 mark
(1) Transition count explanation \rightarrow 1 marks
(2) Syndrome \rightarrow 2 marks
(3) Signature Analysis \rightarrow Block diagram \rightarrow 2 marks
Explanation \rightarrow 2 marks

Total=1+1+2+2+2=8

8 marks

USN	1	P	E							
	<p align="center"> PESIT Bangalore South Campus Hosur road, 1km before Electronic City, Bengaluru -100 Department of Electronics and Communication VLSI Design and Embedded Systems </p>									