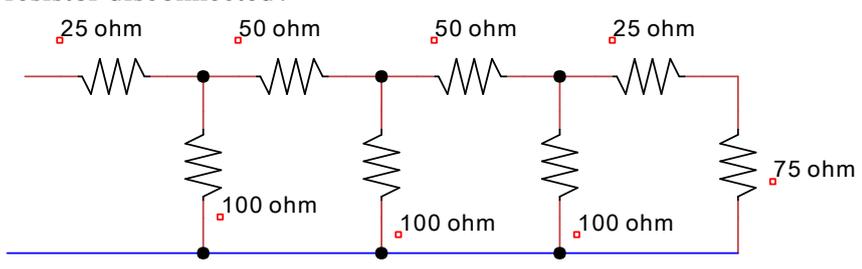
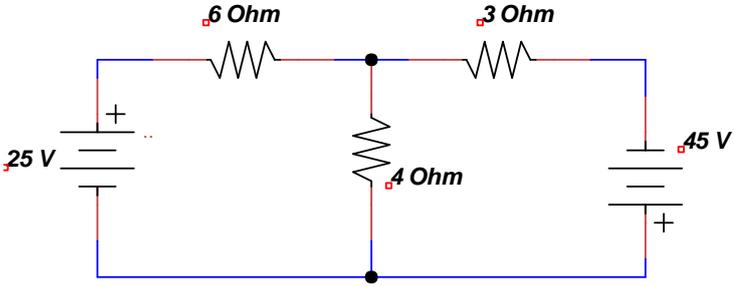
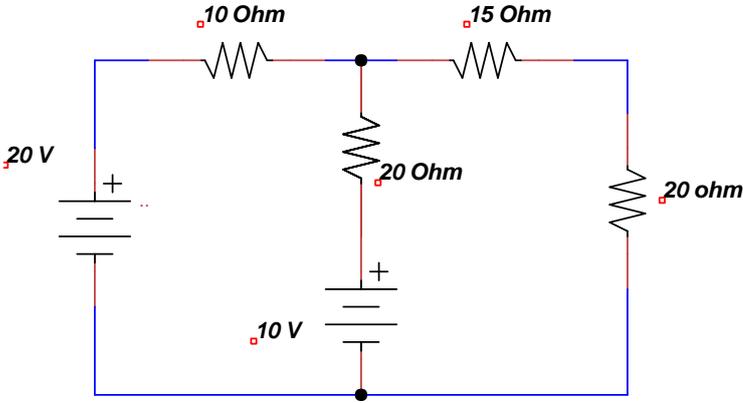


CONTINUOUS INTERNAL EVALUATION TEST -1			
Date : 27/2/2018		Marks:60	
Subject & Code : Basic Electrical Engineering , 17ELE25		Section: A,B,C,D,E	
Name of faculty: Mrs. Dhanashree Bhate, Mr. Prashanth, Mr. Nagendra		Time : 8:30 am – 11:30 a.m	
Note: Answer FIVE full questions choosing any ONE full question from each part.			
PART 1			
1	a	State and explain Ohm's Law and state its limitations	6M
	b	A domestic power load in a house comprises of 8 lamps of 100 W each, 3 fans 80 W each, refrigerator 373 W and a heater 1000 W. Calculate the total current taken from a 230V supply. Calculate energy consumed in a day, if on an average only a quarter of the above load persists all the time.	6M
2	a	State and explain (i) Kirchhoff's Voltage law (ii) Kirchhoff's Current law	6M
	b	What is the equivalent resistance of the ladder network shown in the figure below (i) With 75 Ω load resistor connected as shown (ii) with 75 Ω load resistor disconnected? 	6M
PART 2			
3	a	Define Dynamically and Statically induced emf. Derive the expression for self inductance, $L = \mu_0\mu_r AN^2/l$	6M
	b	Two identical 1000 turns coils X & Y lie in parallel plane such that 60 % of the flux produced by one links the other. A current of 5 A in coil X produces in it a flux of 5×10^{-5} wb. If a current in coil X changes from +6A to -6A in 0.01 sec. What is the EMF induced in coil Y. Calculate the self inductance of each coil and their mutual inductance.	6M
4	a	Derive expression for the coefficient of coupling between two coils and explain the conditions for tightly coupled coils & magnetically isolated coils.	6M
	b	Calculate the self inductance of an air cored solenoid having 25 cm mean diameter, 10cm^2 cross section which is uniformly wound with 1000 turns of wire. Also find the emf induced when a current increasing at the rate of 100 A/sec in winding.	6M
PART 3			
5		Find the current flowing through all the resistances using KCL & KVL. Also find power consumed in all the resistances.	


			
6		<p>Find the current flowing through all the resistances using KCL & KVL. Also find power consumed in all the resistances.</p> 	
PART 4			
7		Define Instantaneous value , maximum value, RMS value and derive the relation between maximum value and RMS value	12M
8		Define phase difference, amplitude of an alternating quantity, average value and derive the relation between the average value and maximum value	12M
PART 5			
9		Prove that the power consumed in an inductor is zero	12M
10		Prove that the power consumed in a capacitor is zero	12M

SCHEME AND SOLUTION
INTERNAL TEST-I

Subject & Code : Basic Electrical Engineering, 14ELE15

Name of faculty: Dhanashree Bhate

Semester: II Section: A,B,C,D,E

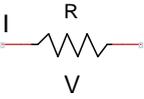Q.No		Marks
1.a	<p>State and explain Ohm's Law and State its limitations</p> <p>Ohm's law : This is the most fundamental law in electrical engineering. It states that the potential difference between two ends of a conductor is directly proportional to the current flowing through it , provided its temperature and other physical parameters remain unchanged .</p> <p style="padding-left: 40px;">That is $V \propto I$ $V=IR$</p> <p>The constant of proportionality R is called resistance of the conductor. The unit is ohm (Ω).The unit ohm is defined as the resistance which permits a flow of one ampere of current when a potential difference of 1 V is applied to the resistance.</p> <div style="text-align: center;">  </div> <p>The resistance R depends on the following factors</p> <p>Length : If the length increases, the distance to be travelled by electrons increases, as the distance increases the electrons will be obstructed by more atoms and molecules present therefore resistance increases with the length.</p> <p style="padding-left: 40px;">ie $R \propto \text{length}$</p> <p>Cross sectional area : If the crosssectional area of conductor increases, the path for flow of electrons increases .Hence opposition offered decreases.</p> <p style="padding-left: 40px;">ie $R \propto 1/\text{crosssectional area}$ $R \propto L/A$ $R = \rho L / A$ where ρ is resistivity of the material $\rho = RA / L$ unit is $\Omega\text{-m}$</p> <p>Limitations :</p> <ol style="list-style-type: none"> This law cannot be applied to unilateral networks. A unilateral network has unilateral elements like diode, transistors, etc., which do not have same voltage current relation for both directions of current. Ohm's law is also not applicable for non – linear elements. Non-linear elements are those which do not have current exactly proportional to the applied voltage, that means the resistance value of those elements changes for different values of voltage and current. Examples of non – linear elements are thyristor, electric arc, etc. 	<p style="text-align: center;">2M</p> <p style="text-align: center;">4M</p>

1.b A domestic power load in a house comprises of 8 lamps of 100 W each, 3 fans 80 W each, refrigerator 373 W and a heater 1000 W. Calculate the total current taken from a 230V supply. Calculate energy consumed in a day, if on an average only a quarter of the above load persists all the time.

$$\begin{aligned} \text{Total power } = P &= 8 \times 100 + 3 \times 80 + 373 + 1000 \\ &= 2413 \text{ watt} \\ &= 2.413 \text{ k W} \end{aligned}$$

3M

$$\begin{aligned} V &= 230 \text{ V and } P = 2413 \text{ watt} \\ \text{Therefore } I &= P/V = 2413/230 = 10.49 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Energy consumed in a day} &= P \times (\text{time}) = 2.413 \times (24) \text{ k W -hr} \\ &= 57.912 \text{ k Watt - hr} \end{aligned}$$

3M


$$\begin{aligned} \text{Energy for } \frac{1}{4} \text{ th load is consumed per day} &= 57.912 \text{ k Watt - hr} \times (0.25) \\ \text{Energy for } \frac{1}{4} \text{ th load is consumed per day} &= 14.478 \text{ k W- hr} \end{aligned}$$

Q.2.a. State and explain (i) Kirchhoff's Voltage law (ii) Kirchhoff's Current law
 Kirchhoff's Current Law :

Statement : Kirchhoff's current law states at any node or a junction the algebraic sum of the currents is zero. $\sum I = 0$.


At node N if I1 & I2 are entering the node and I3 & I4 are leaving from the node then $I1 + I2 - I3 - I4 = 0$

3M

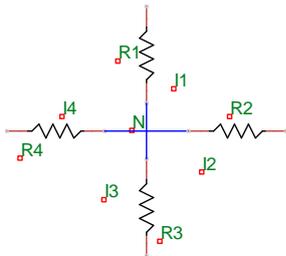

Kirchhoff's Voltage Law :

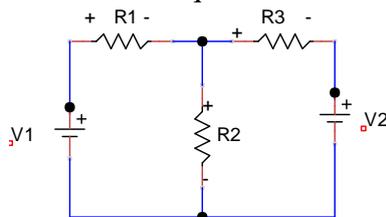
Statement : Kirchhoff's law states that in a closed loop or a mesh the algebraic sum of the voltages is equal to zero. It can be also stated as the sum of the voltage drops in a closed mesh equal to the sum of the voltage gain in the circuit.



3M

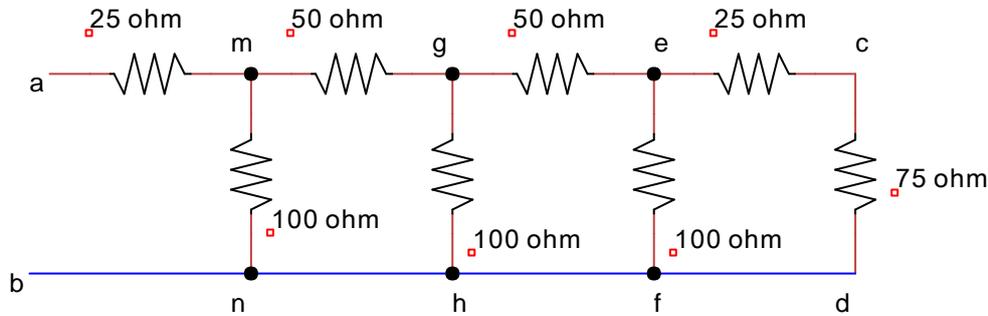Q.2 b.

What is the equivalent resistance of the ladder network shown in the figure below (i) With 75 Ω load resistor connected as shown (ii) with 75 Ω load resistor disconnected?



Let us name the loads and solve

(i) With 75 Ω load resistor connected

$$R_{ef} = 100 \parallel (25 + 75) = 100 \left(\frac{100}{200} \right) = 50 \Omega$$

$$R_{gh} = 100 \parallel (50 + 50) = 50 \Omega$$

$$R_{mn} = 100 \parallel (50 + 50) = 50 \Omega$$

$$R_{ab} = (25 + 50) = 75 \Omega \quad \text{therefore the Req} = 75 \Omega$$

3M

(ii) With 75 Ω load resistor disconnected

When the load of 75 Ω is disconnected, the output terminal c & d become open circuit. the 25 Ω has no effect as no current flows through that part of the circuit hence resistance to the right of nodes g and h

$$R_{gh} = 100 \parallel (50 + 100) = 100 \left(\frac{150}{250} \right) = 60 \Omega$$

resistance to the right of nodes m and n

$$R_{mn} = 100 \parallel (50 + 60) = 100 \left(\frac{110}{210} \right) = 52.4 \Omega$$

This resistance is in series with 25 Ω

$$\text{therefore the Req} = 25 + 52.4 = 77.4 \Omega$$

3M

Q.3.a

Define Dynamically and Statically induced emf. Derive the expression for self inductance, $L = \mu_0 \mu_r AN^2/l$

Emf can be induced in different ways

1. Dynamically induced emf
2. Statically induced emf

Dynamically induced emf


When a magnet is moved towards a coil of N number of turns, the flux linking the coil changes and by Faraday's first law an emf is induced in the coil. This emf is called dynamically induced emf

2M


Statically induced emf

When an ac voltage is applied to the coil, the flux linking with the coil changes with respect to the time. This is called Statically induced emf. There is no movement of

2M

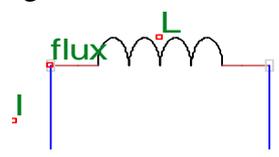	<p>both the coil and the magnet.</p> <p>When current flowing through a coil changes, the flux linking with the coil also changes resulting in an emf called as self induced emf</p> <div style="text-align: center;">  </div> <p>Consider a coil of N turns carrying a current of I A. Let @ be the flux. Flux changes with respect to current in the coil and an emf is induced in the coil. This is called self induced emf and the phenomenon is called as coefficient of self induction. This induced emf opposes the change of current in the coil</p> <p>Derivation:</p> $e \propto di / dt$ $e = L di/dt$ $L = e / di/dt$ <p>But we know that</p> $E = N d\Phi / dt$ <p>Eqauting both the equations</p> $N\Phi = L I$ $L = N\Phi / I$ <p>But flux $\Phi = NI / S$</p> $L = N NI / S I$ $L = N^2 I / l / \mu_0\mu_r A$ $L = \mu_0\mu_r A N^2 / l$ <p>Coefficient of self inductance (L)</p> <p>Coefficient of self inductance L of a coil is defined to be 1 H when the current changes in the coil at the rate of 1A per second inducing an emf of 1V. Unit of self inductance is Henry (H).</p>	<p>2M</p> <p>2M</p> <p>2M</p> <p>2M</p>
Q.3.b	<p>Two identical 1000 turns coils X & Y lie in parallel plane such that 60 % of the flux produced by one links the other. A current of 5 A in coil X produces in it a flux of 5×10^{-5}wb. If a current in coil X changes from +6A to -6A in 0.01 sec. What is the EMF induced in coil Y. Calculate the self inductance of each coil and their mutual inductance.</p> <p>$N_x = 1000$ turns $N_y = 2000$ turns $\Phi_{xy} = 0.6 \Phi_x$ $I_a = 5A$, $\Phi = 5 \times 10^{-5}$wb $dI_x = 12 A$, $dt = 0.01$sec</p>	

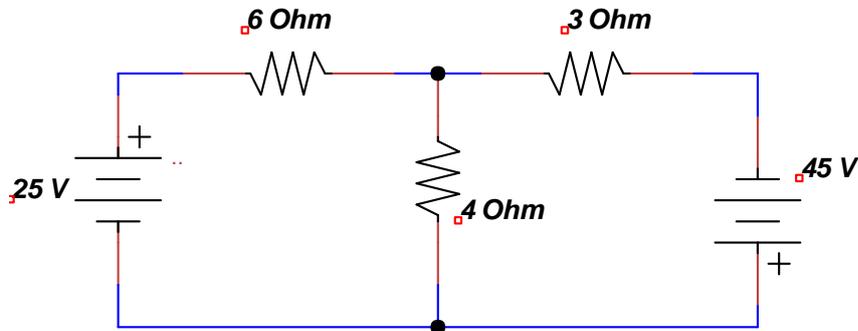Q.5 Find the current flowing through all the resistances using KCL & KVL. Also find power consumed in all the resistances.



Assuming loop current in clockwise direction I_1 in loop 1 ,And I_2 in loop2

Loop 1

$$25 - 6 I_1 - 4 (I_1 - I_2) = 0$$

$$-10 I_1 + 4 I_2 + 25 = 0 \text{ ----- eq 1}$$

Loop 2

$$-3 I_2 + 45 - 4 (I_2 - I_1) = 0$$

$$4 I_1 - 7 I_2 + 45 = 0 \text{ -----eq 2}$$

Solving eq 1 & 2

$$I_1 = 6.57 \text{ A ,}$$

$$I_2 = 10.18 \text{ A}$$

Power consumed in 6Ω $P_1 = (6.57)^2 (6) = 258.98 \text{ watt}$

Power consumed in 3Ω $P_2 = (10.18)^2 (3) = 310.89 \text{ watt}$

Power consumed in 4Ω $P_3 = (3.61)^2 (4) = 52.12 \text{ watt}$


3M

3M

3M

3M

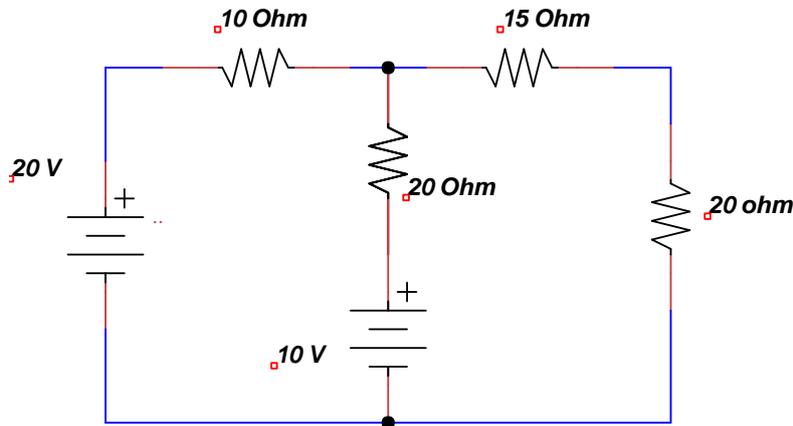Q.6 Find the current flowing through all the resistances using KCL & KVL. Also find power consumed in all the resistances.



Assuming loop current in clockwise direction I_1 in loop 1 ,And I_2 in loop2

Loop 1

$$20 - 10 I_1 - 20 (I_1 - I_2) - 10 = 0$$

$$30 I_1 - 20 I_2 - 10 = 0 \text{ ----- eq 1}$$

Loop 2

$$-35 I_2 + 10 - 20 (I_2 - I_1) = 0$$

$$-20 I_1 + 55 I_2 - 30 = 0 \text{ ----- eq 2}$$

Solving eq 1 & 2

$$I_1 = 0.6 \text{ A}$$

$$I_2 = 0.4 \text{ A}$$

Power consumed in 10Ω $P_1 = (0.6)^2 (10) = 3.6 \text{ watt}$

Power consumed in 15Ω $P_2 = (0.4)^2 (15) = 2.4 \text{ watt}$

Power consumed in 20Ω (middle arm) $P_3 = (0.6-0.4)^2 (20) = 0.8 \text{ watt}$

Power consumed in 20Ω $P_4 = (0.4)^2 (20) = 3.2 \text{ watt}$

3M

3M

3M

3M

Q.7 Define Instantaneous value , maximum value, RMS value and derive the relation between maximum value and RMS value

Instantaneous value:

The magnitude of an alternating quantity at any instant of time is called instantaneous value and denoted by v,i,p

2M


Maximum value :

The maximum value attained by an alternating quantity in every cycle is called the amplitude. The amplitude of voltage or current is denoted by Vm or Im

2M

RMS or effective value: RMS value of an alternating current is defined to be equal to that DC current which produces the same amount of heat as produced by the alternating current when passed through the same resistance for the same time .

2M

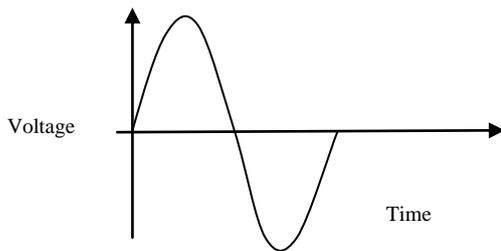

Consider a sinusoidal waveform having equation $E = E_m \sin(\theta)$

4M

The RMS value can be defined as $E_{rms} = \frac{1}{2\pi} \sqrt{\int_0^{2\pi} E_m^2 \sin^2(\theta) d\theta}$

$$= \frac{1}{2\pi} (E_m^2) \sqrt{\int_0^{2\pi} \sin^2(\theta) d\theta}$$

$$= \frac{1}{4\pi} (E_m^2) \sqrt{\int_0^{2\pi} (1 - \cos 2\theta) d\theta}$$

2M


Solving the above equation

$$E_{RMS} = E_m / \sqrt{2}$$

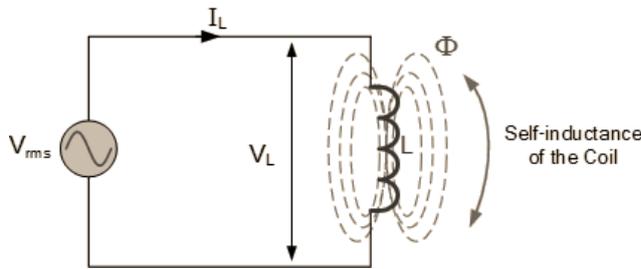Q.9

Prove that the power consumed in an inductor is zero

Consider a circuit with a pure inductor connected to an AC source



Consider a circuit with an inductor L connected across a source of $V = V_m \sin(\omega t)$.

2M

Let I_L be the current flowing through the circuit.

But we know that

$$\begin{aligned} I_L &= \frac{1}{L} \int V dt \\ &= \frac{1}{L} \int V_m \sin(\omega t) dt \\ &= \frac{V_m}{\omega L} (-\cos(\omega t)) \end{aligned}$$


But $X_L = \omega L$ is called inductive reactance of the coil

$$I_L = I_m \sin(\omega t - \pi/2) \text{ -----eq2}$$

$$\text{Where } I_m = \frac{V_m}{X_L}$$

2M

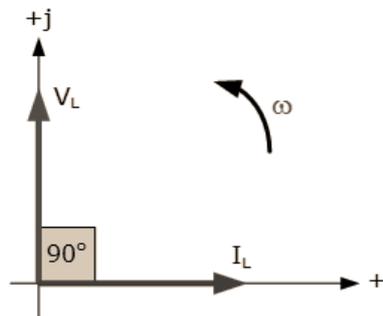Therefore from equation 1 & 2 we can say that the current lags the applied voltage by $\pi/2$



2M

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} p d\omega t$$

2M

$$= \frac{1}{2\pi} \int_0^{2\pi} v \cdot i d\omega t$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) (-I_m \cos(\omega t)) d\omega t$$

$$= -\frac{V_m I_m}{2\pi} \int_0^{2\pi} \sin(\omega t) \cos(\omega t) d\omega t$$

2M

$$= -\frac{V_m I_m}{2\pi} \int_0^{2\pi} \sin \frac{(2\omega t)}{2} d\omega t$$

$$= \frac{V_m I_m}{2\pi} [0]$$


Hence it is proved that the power consumed in an inductor is zero.

$$P_{avg} = 0$$

Power Waveform-----

2M

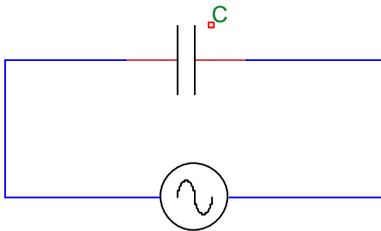Q.10 Prove that the power consumed in a capacitor is zero



$$V = V_m \sin(\omega t)$$

Consider a circuit with a capacitor C connected across a source of $V = V_m \sin(\omega t)$.

Let i be the current flowing through the circuit.

We know that charge $q = CV$

$$\text{Current } i = \frac{dq}{dt}$$

2M

$$i = \frac{dCV}{dt}$$

$$i = \frac{d(CV_m \sin \omega t)}{dt}$$

2M

$$i = C V_m \frac{d(\sin \omega t)}{dt}$$


$$i = (V_m / \omega C) (\cos(\omega t))$$

$$i = (V_m / X_c) \sin(\omega t + \pi/2)$$


$$i = I_m \sin(\omega t + \pi/2)$$

From the above equation we can say that the current leads the applied voltage by $\pi/2$

Waveforms

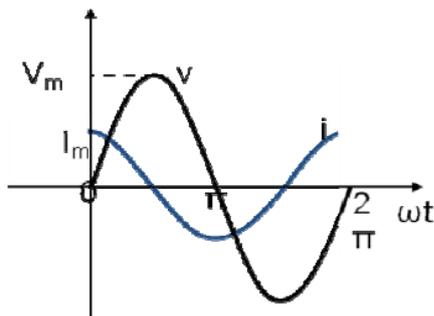

2M

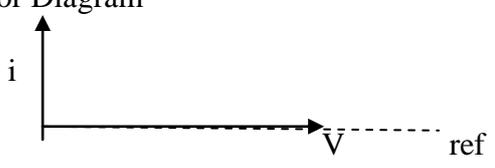	<p>Vector Diagram</p> 	2M
	$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} p \, d\omega t$ $= \frac{1}{2\pi} \int_0^{2\pi} v \cdot i \, d\omega t$ $= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) I_m \cos(\omega t) \, d\omega t$ $= \frac{V_m I_m}{2\pi} \int_0^{2\pi} \sin(\omega t) \cos(\omega t) \, d\omega t$ $= \frac{V_m I_m}{2\pi} \int_0^{2\pi} \sin\left(\frac{2\omega t}{2}\right) \, d\omega t$ $= \frac{V_m I_m}{2\pi} [0]$	2M
	<p>$P_{avg} = 0$</p> <p>Hence it is proved that the power consumed in a capacitor is zero</p>	
	<p>Power Waveform-----</p>	2M



PESIT Bangalore South Campus
Hosur road, 1km before Electronic City, Bengaluru -100
Department of Electronics & Communication Engineering

--	--	--